

KAMARAJ COLLEGE (Autonomous)

Accredited with A+ Grade by NAAC

(Affiliated to Manonmaniam Sundaranar University, Tirunelveli)

THOOTHUKUDI – 628 003

(5 Pages)

Reg. No:

Question Code No : 250003310

Course Code : 24PEPH14

PG Degree - End Semester Examinations, November 2025

First Semester

M.Sc. PHYSICS

Linear and Digital ICS and Applications

(For those who joined in July 2024 onwards)

Time : 3Hours

Maximum : 75 Marks

PART – A (10 × 1 = 10 Marks)

Answer ALL Questions

Choose the correct answer :

1. Which IC is commonly used as a general-purpose operational amplifier?
(a) IC 565 (b) IC 723
(c) IC 741 (d) IC 555
2. In an inverting op-amp, the input is applied to
(a) Non-inverting terminal (b) Output

- (c) Inverting terminal (d) Both terminals
3. Instrumentation amplifier is primarily used for
- (a) High common-mode (b) High power output
rejection ratio
- (c) Low input impedance (d) High current gain
4. Which filter provides constant gain over a pass band?
- (a) Band-stop filter (b) All-pass filter
- (c) Butterworth filter (d) High-pass filter
5. An all-pass filter is mainly used for
- (a) Attenuating noise (b) Power amplification
- (c) Frequency selection (d) Phase correction
6. A Schmitt trigger is mainly used for
- (a) Amplifying low-level (b) Removing noise and
signals providing hysteresis
- (c) Converting analog to (d) Generating sine waves
digital
7. Which regulator offers high efficiency due to rapid switching
action?
- (a) Zener diode regulator (b) Linear series regulator
- (c) Switching regulator (d) IC 723 regulator
8. The dual slope ADC is preferred in digital voltmeters because
of

- (a) High resolution and noise rejection (b) Low power supply requirement
(c) High conversion speed (d) Simplicity of design

9. The IC 7447 is commonly used as

- (a) Flip-flop (b) Multiplexer
(c) BCD to 7-segment decoder (d) Encoder

10. The IC used for 7-segment decoding is

- (a) IC 74194 (b) IC 7447
(c) IC 7473 (d) IC 7483

PART - B (5 X 5 = 25 Marks)

Answer ALL Questions choosing either (a) or (b).

Answer should not exceed 250 words.

11. (a) List the characteristics of an ideal op-amp.

(OR)

(b) Discuss the DC characteristics of the IC 741 op-amp.

12. (a) Describe the construction and working of an instrumentation amplifier.

(OR)

(b) Explain the function of a Schmitt trigger circuit.

13. (a) Draw the circuit of an all pass filter and explain its working.

(OR)

(b) With a neat diagram, explain the functional block diagram of the 555 timer IC.

14. (a) List and explain the characteristics of three terminal IC voltage regulator.

(OR)

(b) In an inverted R-2R ladder DAC with $R = R_f = 10k\Omega$ and $V_R = 10V$, Calculate the output voltage for the binary output of 1110.

15. (a) Write short notes on CMOS NAND and NOR gates.

(OR)

(b) Explain the working of IC 7493 as a 4-bit asynchronous binary counter.

PART – C (5 X 8 = 40 Marks)

Answer ALL Questions choosing either (a) or (b).

Answer should not exceed 600 words.

16. (a) With a neat diagram, explain the internal circuit of op-amp 741 and highlight its features.

(OR)

(b) Explain in detail the inverting and non-inverting mode of operation.

17. (a) Draw and explain the operation of V to I and I to V converter.

(OR)

(b) With a circuit diagram, explain the working principle of square wave generator.

18. (a) With circuit diagram, explain the working of second-order Butterworth low-pass filter.

(OR)

(b) List the applications of PLL and explain any two with diagrams.

19. (a) Explain the working of IC 723 as a general-purpose regulator.

(OR)

(b) Explain the operation of dual slope ADC.

20. (a) Explain the design and operation of a universal shift register (IC 74194).

(OR)

(b) Discuss the working of IC 7485 comparator and IC 7447 BCD to 7-segment decoder.