

(6 pages)

Reg. No. : .....

Code No. : 30454 E Sub. Code : CMPH 51

B.Sc. (CBCS) DEGREE EXAMINATION,  
NOVEMBER 2024.

Fifth Semester

Physics — Core

BASIC ELECTRONICS

(For those who joined in July 2021 and 2022 only)

Time : Three hours

Maximum : 75 marks

PART A — (10 × 1 = 10 marks)

Answer ALL questions.

Choose the correct answer :

1. If a signal passed through an integrator, it ——— the amplitude of noise signal.  
(a) Enhance (b) Factorizes  
(c) Stabilizes (d) Reduces
2. The ripple voltage of a full-wave rectifier with a 100  $\mu$ F filter capacitor connected to a load drawing 50 mA is  
(a) 2.4 kV (b) 1.8 kV  
(c) 4.8 kV (d) 1.2 kV

3. Hartley oscillator is a ———

- (a) Phase shift oscillator
- (b) RC oscillator
- (c) Crystal oscillator
- (d) LC oscillator

4. Oscillator operate on the principle of ———

- (a) Positive feedback (b) Negative feedback
- (c) Signal feedthrough (d) Attenuation

5. Multi-vibrators can be used to produce which type of signals ———

- (a) Triangular wave (b) Impulse
- (c) Sine wave (d) Square wave

6. An integrator contains a 100 kilo ohms and 1  $\mu$ F capacitor. If the voltage applied to the integrator input is 1V, what is the voltage present at the integrator output after 1s?

- (a) 1V (b) 5V
- (c) 2V (d) 10V

7. If a capacitor is placed in the feedback path of an op-amp circuit, then the circuit can act as ———

- (a) Integrator                      (b) Multiplier  
(c) Subtractor                      (d) None of the above

8. An op-amp as a voltage follower has a voltage gain of ———

- (a) Infinity                      (b) Zero  
(c) Unity                      (d) Negative value

9. The maximum efficiency of a half-wave rectifier is ———

- (a) 50.6%                      (b) 40.6%  
(c) 81.2%                      (d) 40.2%

10. If the input to differentiating circuit is a sawtooth wave, then the output will be ——— wave.

- (a) Square                      (b) Rectangular  
(c) Triangular                      (d) None of these

PART B — (5 × 5 = 25 marks)

Answer ALL questions choosing either (a) or (b).  
Each answer should not exceed 250 words.

11. (a) Discuss about the Norton's theorem.

Or

(b) Explain the h parameters of a transistor.

12. (a) Explain the Tunnel diode.

Or

(b) Discuss about the zener diode.

13. (a) Describe the push pull amplifier.

Or

(b) Explain the construction and working function of class B power amplifier.

14. (a) Discuss about the clipping and clamping circuits.

Or

(b) Explain the construction and working of monostable multivibrator.

15. (a) Describe the adder and subtractor circuits.

Or

- (b) What are the characteristics of ideal operational amplifier?

PART C — (5 × 8 = 40 marks)

Answer ALL questions choosing either (a) or (b).  
Each answer should not exceed 600 words.

16. (a) Explain the conversion of voltage source into current source.

Or

- (b) Define the h parameter and explain the thevenin's theorem.

17. (a) Explain the construction and working function of tap full wave rectifier.

Or

- (b) Explain the construction and working function of Half wave rectifier.

18. (a) Discuss about the class A and class C power amplifier.

Or

- (b) Explain the construction and working function of common emitter and common collector transistor.

19. (a) Explain the construction and working function of Astable multivibrator using transistor.

Or

- (b) Discuss about the Hartely oscillator.

20. (a) Explain the low pass and high pass filters.

Or

- (b) Describe the inverting and non inverting amplifier.