

4. $x + xy =$ _____
 (a) y (b) 1
 (c) 0 (d) x
5. The 2's complement of 1011000 is _____
 (a) 0100111 (b) 0010100
 (c) 1001001 (d) 1010010
6. The binary subtraction of two number to produces result as _____
 (a) 10 (b) 11
 (c) 1 (d) 0
7. Find the odd one out _____
 (a) RS flipflop (b) JP flipflop
 (c) D flipflop (d) Master slave flipflop
8. A group of flip-flops sensitive to pulse is called a _____
 (a) Resister (b) Gate
 (c) Catch (d) Decoder
9. MRI stands for _____
 (a) Memory Reference Instruction
 (b) Memory Register Instruction
 (c) Memory Reference Integration
 (d) Memory Register Instruction
10. Ripple counter is _____ counter.
 (a) Synchronous (b) Asynchronous
 (c) Serial (d) Parallel

PART B — (5 × 5 = 25 marks)

Answer ALL questions, choosing either (a) or (b).

11. (a) Do the following :
 (i) Convert $(0.6875)_{10}$ to binary
 (ii) Convert $(0.513)_{10}$ to octal.
 Or
 (b) Which gates are called a universal logic gates? Why?
12. (a) What is a constructor? Write down the characteristics of constructor function.
 Or
 (b) Write short notes on : Encoders.
13. (a) Explain the features of Member functions.
 Or
 (b) Discuss in detail 2's complement arithmetic with examples.
14. (a) Discuss the principle of clocked RS flipflops.
 Or
 (b) What is D flip-flop? Explain.
15. (a) Write about serial in-parallel out shift register.
 Or
 (b) What are the types of registers? Explain.