

PART A - (10 × 1 = 10 marks)

Answer ALL questions.

Choose the correct answer.

1. What is the decimal equivalent of (1101)₂?
(a) 13 (b) 11
(c) 1011 (d) 19
2. Which code is used to send digital data over telephone lines
(a) BCD (b) GRAY code
(c) ASCII (d) EBCDIC

3. $AB + \bar{A}C + BC =$ _____
(a) $(A + B)(\bar{A} + C)$ (b) $AB + \bar{A}C$
(c) $AB + BC$ (d) $\bar{A}C + BC$
4. How many fundamental products are there for four variables?
(a) 2 (b) 4
(c) 8 (d) 16
5. $A \oplus B =$ _____
(a) $A + B$ (b) $AB + \bar{A}\bar{B}$
(c) $A\bar{B} + \bar{A}B$ (d) $\bar{A} + \bar{B}$
6. 2's complement of $(-96)_{10}$ is _____
(a) 11100000 (b) 10100000
(c) 01010000 (d) 01001111
7. In S - R flip-flop, if $Q = 0$ the output is said to be _____
(a) Set (b) Reset
(c) Previous state (d) Current state
8. In which flip-flop output follows the input?
(a) RS (b) D
(c) JK (d) T

Page 2 Code No. : 10754 E

9. Which of the following flip flop is not used to construct registers?
(a) RS (b) D
(c) JK (d) T
10. In parallel shift registers, data shifting occurs _____
(a) 1 bit at a time (b) Simultaneously
(c) Two bit at a time (d) Four bit at a time

PART B - (5 × 5 = 25 marks)

Answer ALL questions by choosing (a) or (b).

Each answer should not exceed 250 words.

11. (a) (i) Convert binary 110.001 to a decimal number.
(ii) If a 16 bit number has all 1s, what is its decimal equivalent?
Or
(b) Write a note on Graycode.
12. (a) Write the consensus theorem.
Or
(b) What is the simplified Boolean equation for the following logic equation?
 $F(A, B, C, D) = \sum m(7, 9, 11, 12, 13, 14, 15)$

Page 3 Code No. : 10754 E

13. (a) Write a note on multiplexer.
Or
(b) Perform binary addition $(-43)_{10}$ and $(-78)_{10}$.
14. (a) Write a note on RS flip flop.
Or
(b) Write a note on edge triggered D flip flop.
15. (a) Give the sketch of serial in parallel out register.
Or
(b) Give the sketch of parallel in parallel out register.

PART C - (5 × 8 = 40 marks)

Answer ALL questions by choosing (a) or (b).

Each answer should not exceed 600 words.

16. (a) Tabulate the BCD representation and Excess-3 code for Decimal 0 - 9.
Or
(b) Explain the universal logic gates.

Page 4 Code No. : 10754 E

17. (a) Construct the truth table for
(i) two input NOR gate
(ii) three input Ex-OR gate

Or

- (b) Convert the following truth table to Karnaugh map and draw logic circuit.

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

18. (a) Subtract $(-43)_{10}$ and $(-78)_{10}$ in binary form.

Or

- (b) Explain 7 segment decoder.

19. (a) Explain edge triggered RS flip flop

Or

- (b) Explain JK Master-Slave flipflop.

20. (a) Explain serial in parallel out register.

Or

- (b) Explain universal shift register.